


# HURRAY!

**The FINAL step for building the PocketPAL kit is finally here!**


It has been a long journey of flooded basements, lost prototypes, dead laptop, clones that were not clones and a ton of other unexpected stuff. Anyway, I finally was able to coax my 18 year old laptop into limping along long enough to search for some long lost PAL files. Combined with some new-found notes, the reappearance of the long lost prototypes and a week of debugging and programming, I finally got the prototype to do what I intended it to do when I started the project many years ago. There are a few modifications that need to be done in order to make the circuitry function properly. They are noted in RED on the schematic so you need to study the schematic carefully.




MODs required:

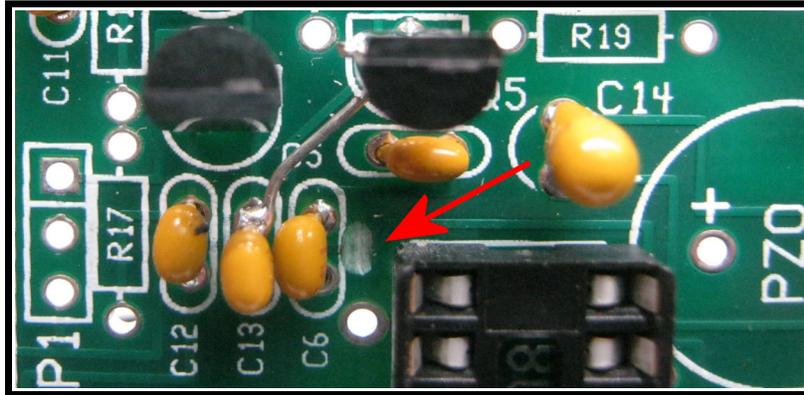

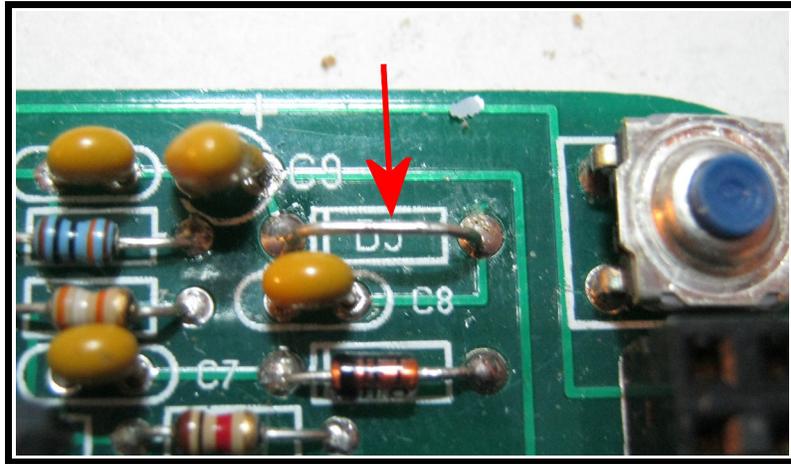
1. Cut the +5V feed to the collector of Q5 where it passes around U1, the Picaxe micro. Just to the left of the DIP socket, the trace passes underneath C6 and then on to the collector of Q5.



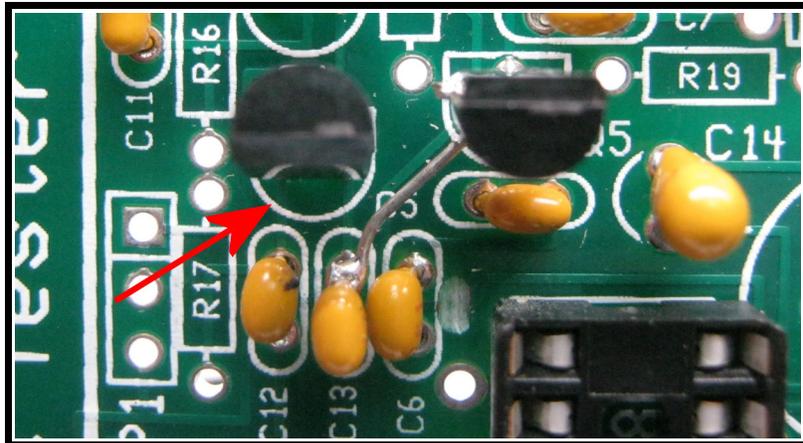
2. D5, a 1N4148 transistor, is not required so install a shorting jumper between the D5 pads instead of a diode.



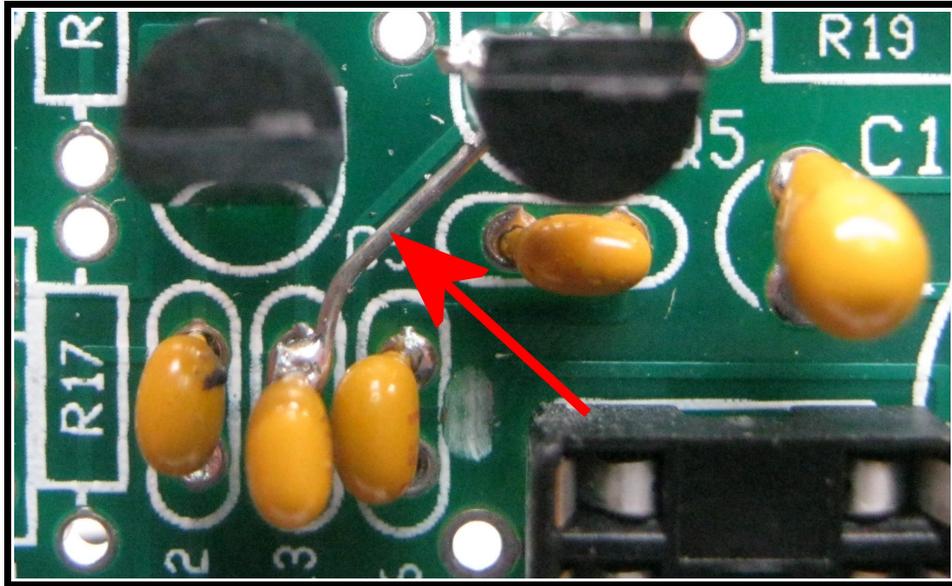3. The silk screen designator for Q4, the 2N4403 transistor, is backwards. When called for, install Q4 backwards from the silk screen.



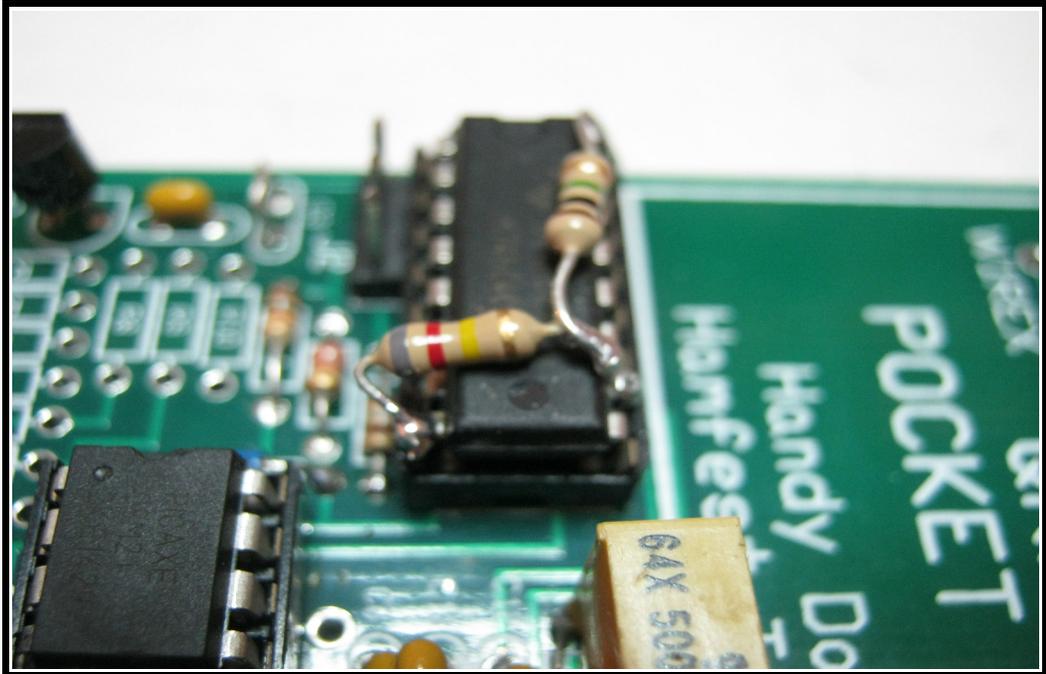4. When assembling the last stage, install Q2 and C13 first, with about 1/4" of component leads above the board. Then you use a short piece of cut off component lead to make a connection between C13 and Q5 as shown on the schematic. This mod will now cause the oscillator to generate a larger voltage swing on the output signal before it heads on to the signal shaping circuit.



5. A pair of biasing resistors are required for the ripple counter chip to clock properly. I soldered them VERY carefully directly to the pins of the counter chip.
  
6. When in operation, the trimmer potentiometer needs to be adjusted so that the output signal of the shaper circuit, comprised by Q3 & Q4, has a signal level high enough to create the clock pulses into the ripple counter. Once adjusted properly, the ripple counter takes the full oscillator frequency And divides it by 1024 thereby creating a signal slow enough to be counted by the Picaxe Count command. A 7030 crystal oscillates at approx 7,030,000 which goes into the ripple counter which then outputs a divided by 1024 frequency of 6865 Hz. The Picaxe program now needs to do a little math before reporting the crystal frequency....

The order of assembly steps that I did to finish my PAL were:

1. Cut the switched +5V trace just left of pin5 of the IC socket.
2. Install the 2N2222 transistor at Q5 and a .1uf cap at C13 keeping them about 1/4" up off the pcb.
3. Use a piece of clipped component lead to connect the +9V end of C13 to the collector of Q5.
4. Solder in the 16 pin IC socket for the counter chip.
5. Check the capacitor values and install the remaining capacitors: C5, C6, C7, C8, C9, C10, C11, and C12.
6. Solder in the resistors: R14, R15, R16, R17, R18 and R19
7. Now install diodes: D1, D2, D4 and a shorting wire across D5.
8. Solder in the MPF102 transistor at Q3.
9. Install the 2N4403 at Q4 transistor making sure you install it OPPOSITE the silk screen designator.
10. CAREFULLY solder the 820K resistor directly onto the 4020 counter chip between pins 8 & 10.
11. Again CAREFULLY, solder the 1M resistor directly between pins 10 & 16 of the 4020 chip.
12. Insert the modified 4020 counter IC into the 16 pin socket.

The counter circuit won't function properly unless the trimmer pot is properly adjusted. The proper trimmer setting will create a maximum signal level into the biased input of the counter chip. The biasing resistors set the DC level at the clock input of the 4020 right in the middle of the signal logic levels for 0 and 1 logic levels. Then the amplified level from the oscillator and shaper circuits is AC coupled onto the clock input creating a clock signal to the 4020 at the crystal frequency. The 4020 divides that rf

frequency by 1024 creating an output signal below 25Khz which is the maximum frequency countable by the Count command in the Picaxe. Therefor, the maximum frequency of a crystal that can be measured with the Pocket PAL is 25Mhz.

Your handy dandy PocketPAL tester should now output a 4 or 5 digit frequency in Morse Code when you power the tester up with a crystal in the XTAL socket. Without a crystal in the XTAL socket, the PocketPAL will sound AUDIO test tones on the INTERNAL piezo signal and also send those audio tones out the test connector to a piezo or speaker plugged into the test socket..

The Picaxe PocketPAL programs up on the site will complete your build AND provide the above functionality.

Hope everything works out for you.

If you have already installed the 2N4403 transistor and need to yank it out, you will probably not be able to save it for reuse. I had to change mine.... It is much easier to simply give up on trying to save it and just take it out and replace it with a new one. The 4020 biasing resistors are new to the design so you need to source those too. I will supply them for FREE to anyone who needs them for their PAL kits.